EE4-18
EE9-AO6

IMPERIAL COLLEGE LONDON

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
EXAMINATIONS 2021

MSc and EEE PART IV: MEng and ACGI

RADIO FREQUENCY ELECTRONICS

Friday, 14 May 10:00 am

Time allowed: 3:00 hours

There are SIX questions on this paper.

Answer FOUR questions.

All questions carry equal marks

Any special instructions for invigilators and information for candidates are on page 1.

Examiners responsible First Marker(s) : S. Lucyszyn
Second Marker(s) : W.T. Pike

© Imperial College London

Special instructions for invigilators

This is an open book examination.

Special instructions for students

All variables have their usual meaning.

Standard filter curves and tables are given after the questions.

The Questions

1.

a) Consider a ‘Fibre Radio’ communications system:

i) Illustrate and briefly explain the basic concept.

[2]

ii) What is the main reason for introducing this technology?

[1]

iii) Briefly explain the reasons why its implementation has not been successful.

[1]

b) Draw the basic block diagram for a high-speed optical communications system, clearly indicating all the blocks.

[3]

c) For the implementation in 1(b):

i) What is the main systems-level challenge?

[1]

ii) What is the main circuit-level challenge?

[1]

iii) With suitable examples, briefly explain the transistor technology choice as data rates increase from 10 Gb/s to 40 Gb/s.

[2]

d) For a typical optical driver in 1(b):

i) Input and output voltages are 0.4 $V_{pk\text{-}pk}$ and 8 $V_{pk\text{-}pk}$, respectively, and it consumes 2.5 W of DC power. With an output power of 20 dBm, calculate the gain in dB and basic output efficiency for this power amplifier.

[3]

ii) Briefly explain why an ‘all transistor’ solution is needed and how this differs from a conventional MMIC amplifier circuit design.

[2]

iii) With the use of illustration(s), explain why extreme RF decoupling is needed and how it is realized in the biasing circuitry.

[4]

2.

a) Draw the basic circuit diagram for a 4-stage distributed amplifier (also known as the travelling-wave amplifier). Describe the basic principle of operation and from this state its main advantage over traditional amplifiers.

[5]

b) Given identical FETs, represented by a simple equivalent circuit model having intrinsic values of C_{gs} = 1 pF, C_{ds} = 0.5 pF and g_m = 100 mS, calculate the inductance values and cut-off frequency for a 50 Ω input gate transmission line. Also, for a 4-stage distributed amplifier, calculate the available power gain. For a constant-K ladder network, the phase velocity per section is given by Equation (2.1) and the available power gain is given by Equation (2.2):

$$Phase\ Velocity/Section = \frac{1}{\sqrt{LC}} \tag{2.1}$$

$$Available\ Power\ Gain = \left(\frac{N g_m \sqrt{Z_{og} Z_{od}}}{2}\right)^2 \tag{2.2}$$

where N is the number of stages, g_m is the transconductance and Z_{og} and Z_{od} are the characteristic impedances for the input gate and output drain transmission lines, respectively.

[5]

c) Explain why the gain-bandwidth product does not theoretically change if the size of the transistors in 2(b) is doubled. Also, explain why more stages do not necessarily give more power gain.

[5]

d) From the photograph in Figure 2.1, using deduction, draw the equivalent circuit model.

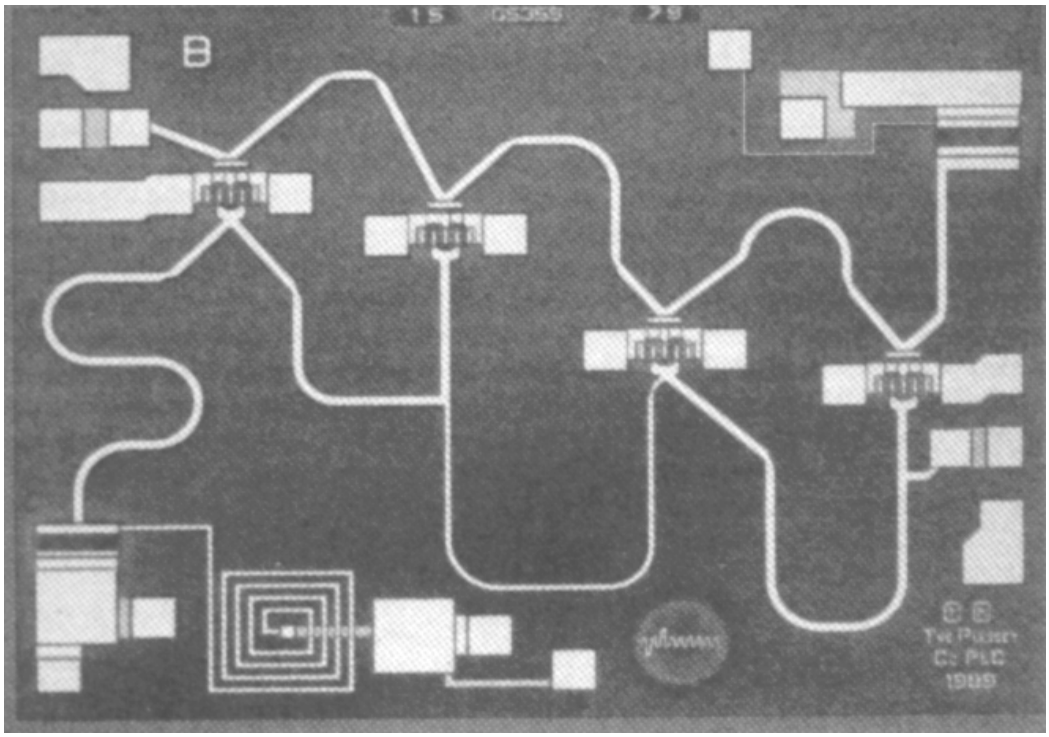


Figure 2.1 Photograph of an MMIC.

[5]

3. Consider a two-stage 1 W amplifier. It consists of a driver and power amplifier (PA), having specifications given in Table 2.1:

Specifications	Driver	Power Amplifier
Power Gain (dB)	10	3
DC Power (W)	1	2.5
1 dB Gain Compression Point (dBm)	27	27
Noise Figure (dB)	2	3
Input and Output Impedances (Ω)	50	50
Third-order Intercept Point (dBm)	50	40

Table 2.1

a) With the normal driver-PA configuration, calculate:

i) Overall gain.

[1]

ii) Overall basic output efficiency and PAE.

[3]

iii) Overall noise figure.

[2]

iv) Overall IP3.

[2]

b) With the PA mistakenly feeding the driver, calculate:

v) Overall gain.

[1]

vi) Overall basic output efficiency and PAE.

[3]

vii) Overall noise figure.

[2]

viii) Overall IP3.

[2]

c) Comment on the output power levels for both stages, relative to P_{1dB}, with both 3(a) and 3(b). What would you expect the power gain to do with each stage in 3(b)?

[3]

d) With 3(b), is the basic output efficiency of the second stage practical and if not state why?

[1]

4.

a) An ideal four-port coupled-line directional coupler has the following S-parameters: $S_{21} = 0.6$ to its coupled port and $S_{41} = -j0.8$ to its direct port. Draw a symbolic representation of this coupler, labelling the appropriate port numbers. By inspection, write down the complete S-parameter matrix for this coupler, identifying all assumptions about losses, symmetry and reciprocity.

[4]

b) Using the symbolic representation for the ideal coupler in 4(a), draw the circuit schematic for an ideal three-port Marchand balun, labelling the port numbers.

[3]

c) By inspection of 4(b), derive the expression of S_{21} for the balun and calculate this coefficient. The following general mathematical relationship should be used to represent infinite reflections between two impedance boundaries:

$$\sum_{i=0}^{\infty} A^i = \frac{1}{1-A} \tag{4.1}$$

[6]

d) By inspection of 4(b), derive the expression of S_{31} for the balun and calculate this coefficient. The same use of Equation (4.1) will be needed. Using the results here and from 4(c), confirm that this circuit operates as a balun.

[4]

e) By inspection of 4(b), derive the expression of S_{11} for the balun and calculate the input return loss. The same use of Equation (4.1) will be needed.

[3]

5. Consider a transistor having the following small-signal matrix, S, at 2.45 GHz:

$$\begin{pmatrix} 0.5\angle -150° & 0.2\angle +20° \\ 20\angle +85° & 0.4\angle +30° \end{pmatrix}$$

a) Calculate the maximum unilateral transducer power gain, given by Equation (5.1):

$$G_{TU_max} = \frac{1}{1-|S_{11}|^2} |S_{21}|^2 \frac{1}{1-|S_{22}|^2} \quad (5.1)$$

[4]

b) Using textbook equations, calculate the Rollet stability factor. Is the amplifier unconditionally or conditionally stable and why?

[6]

c) Depending on your answer in 5(b), using textbook equations, calculate either the maximum stable gain or maximum available gain in dB. How does this compare with the value in 5(a)?

[4]

d) The input impedances looking into the transistor is 49.0 - j8.25 Ω. Using discrete elements, design a two-element impedance matching network. What is the ideal -3 dB bandwidth of this input matching stage?

[6]

6. The 802.11 b/g/n Wi-Fi allocated spectrum is from 2401 MHz to 2484 MHz.

a) Block out the 802.11 b/g/n Wi-Fi signal by designing a suitable 5th-order Chebyshev filter, having a worst-case passband ripple of 1 dB, with shunt-first element and 50 Ω port terminations.

[14]


b) With the design in 6(a), what is the level of attenuation at the band edges and at 2421.75 MHz?

[3]


c) Calculate the worst-case level of passband return loss?

[3]


Standard Filter Curves and Tables

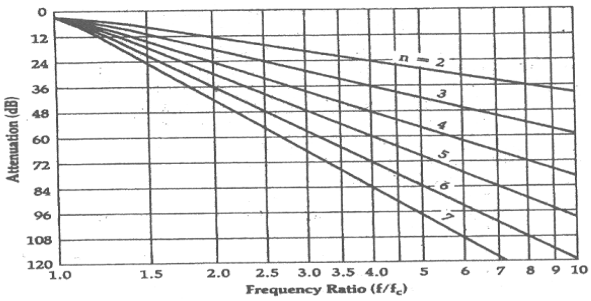

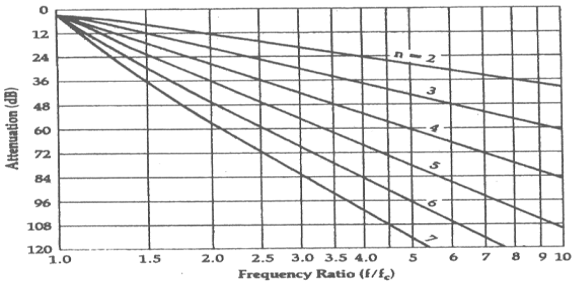
Attenuation characteristics for Butterworth filters.



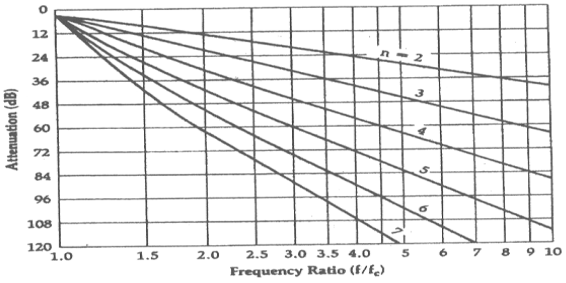
Attenuation characteristics for a Chebyshev filter with 0.01-dB ripple.



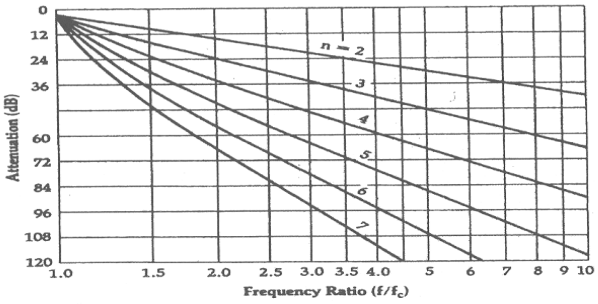Attenuation characteristics for a Chebyshev filter with 0.1-dB ripple.




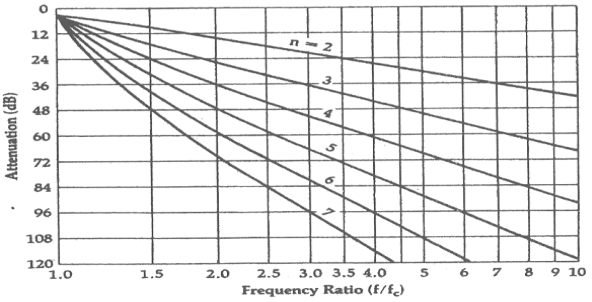Attenuation characteristics for a Chebyshev filter with 0.5-dB ripple.




Attenuation characteristics for a Chebyshev filter with 1-dB ripple.

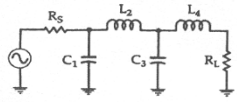Chebyshev Low-Pass Prototype Element Values for 1.0-dB Ripple




R_S/R_L	C_1	L_2	C_3	L_4
3.000	0.572	3.132		
4.000	0.365	4.600		
8.000	0.157	9.658		
∞	1.213	1.109		
1.000	2.216	1.088	2.216	
0.500	4.431	0.817	2.216	
0.333	6.647	0.726	2.216	
0.250	8.862	0.680	2.216	
0.125	17.725	0.612	2.216	
∞	1.652	1.460	1.108	
3.000	0.653	4.411	0.814	2.535
4.000	0.452	7.083	0.612	2.848
8.000	0.209	17.164	0.428	3.281
∞	1.350	2.010	1.488	1.106

R_L/R_S	L_1	C_2	L_3	C_4

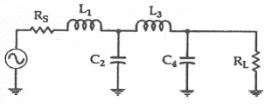


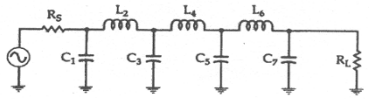Chebyshev Low-Pass Prototype Element Values for 1.0-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	1.000	2.207	1.128	3.103	1.128	2.207		
	0.500	4.414	0.565	4.653	1.128	2.207		
	0.333	6.622	0.376	6.205	1.128	2.207		
	0.250	8.829	0.282	7.756	1.128	2.207		
	0.125	17.657	0.141	13.961	1.128	2.207		
	∞	1.721	1.645	2.061	1.493	1.103		
6	3.000	0.679	3.873	0.771	4.711	0.969	2.406	
	4.000	0.481	5.644	0.476	7.351	0.849	2.582	
	8.000	0.227	12.310	0.198	16.740	0.726	2.800	
	∞	1.378	2.097	1.690	2.074	1.494	1.102	
7	1.000	2.204	1.131	3.147	1.194	3.147	1.131	2.204
	0.500	4.408	0.566	6.293	0.895	3.147	1.131	2.204
	0.333	6.612	0.377	9.441	0.796	3.147	1.131	2.204
	0.250	8.815	0.283	12.588	0.747	3.147	1.131	2.204
	0.125	17.631	0.141	25.175	0.671	3.147	1.131	2.204
	∞	1.741	1.677	2.155	1.703	2.079	1.494	1.102

n	R_L/R_S	L_1	C_2	L_3	C_4	L_5	C_6	L_7

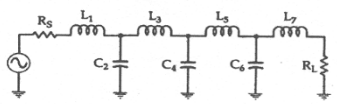


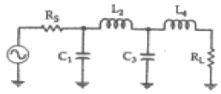Butterworth Low-Pass Prototype Element Values




n	R_S/R_L	C_1	L_2	C_3	L_4
2	1.111	1.035	1.835		
	1.250	0.849	2.121		
	1.429	0.697	2.439		
	1.667	0.566	2.828		
	2.000	0.448	3.346		
	2.500	0.342	4.095		
	3.333	0.245	5.313		
	5.000	0.156	7.707		
	10.000	0.074	14.814		
	∞	1.414	0.707		
3	0.900	0.808	1.633	1.599	
	0.800	0.844	1.384	1.926	
	0.700	0.915	1.165	2.277	
	0.600	1.023	0.965	2.702	
	0.500	1.181	0.779	3.261	
	0.400	1.425	0.604	4.064	
	0.300	1.838	0.440	5.383	
	0.200	2.669	0.284	7.910	
	0.100	5.167	0.138	15.455	
	∞	1.500	1.333	0.500	
4	1.111	0.466	1.592	1.744	1.469
	1.250	0.388	1.695	1.511	1.811
	1.429	0.325	1.862	1.291	2.175
	1.667	0.269	2.103	1.062	2.613
	2.000	0.218	2.452	0.883	3.187
	2.500	0.169	2.986	0.691	4.009
	3.333	0.124	3.883	0.507	5.338
	5.000	0.080	5.684	0.331	7.940
	10.000	0.039	11.094	0.162	15.642
	∞	1.531	1.577	1.062	0.383

n	R_L/R_S	L_1	C_2	L_3	C_4

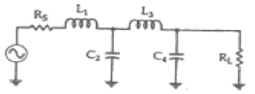


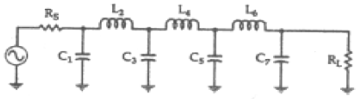Butterworth Low-Pass Prototype Element Values




n	R_S/R_L	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	0.900	0.442	1.027	1.910	1.756	1.389		
	0.800	0.470	0.866	2.061	1.544	1.738		
	0.700	0.517	0.731	2.285	1.333	2.108		
	0.600	0.586	0.609	2.600	1.126	2.552		
	0.500	0.686	0.496	3.051	0.924	3.133		
	0.400	0.838	0.388	3.736	0.727	3.965		
	0.300	1.094	0.285	4.884	0.537	5.307		
	0.200	1.608	0.186	7.185	0.352	7.935		
	0.100	3.512	0.091	14.095	0.173	15.710		
	∞	1.545	1.694	1.382	0.894	0.309		
6	1.111	0.289	1.040	1.322	2.054	1.744	1.335	
	1.250	0.245	1.116	1.126	2.239	1.550	1.688	
	1.429	0.207	1.236	0.957	2.499	1.346	2.062	
	1.667	0.173	1.407	0.801	2.858	1.143	2.509	
	2.000	0.141	1.653	0.654	3.369	0.942	3.094	
	2.500	0.111	2.028	0.514	4.141	0.745	3.931	
	3.333	0.082	2.656	0.379	5.433	0.552	5.280	
	5.000	0.054	3.917	0.248	8.020	0.363	7.922	
	10.000	0.026	7.705	0.122	15.786	0.179	15.738	
	∞	1.553	1.759	1.553	1.202	0.758	0.259	
7	0.900	0.299	0.711	1.404	1.489	2.125	1.727	1.296
	0.800	0.322	0.606	1.517	1.278	2.334	1.546	1.652
	0.700	0.357	0.515	1.688	1.091	2.618	1.350	2.028
	0.600	0.408	0.432	1.928	0.917	3.005	1.150	2.477
	0.500	0.480	0.354	2.273	0.751	3.553	0.951	3.064
	0.400	0.590	0.278	2.795	0.592	4.380	0.754	3.904
	0.300	0.775	0.206	3.671	0.437	5.761	0.560	5.258
	0.200	1.145	0.135	5.427	0.287	8.526	0.369	7.908
	0.100	2.257	0.067	10.700	0.142	16.822	0.182	15.748
	∞	1.558	1.799	1.659	1.397	1.055	0.656	0.223

n	R_L/R_S	L_1	C_2	L_3	C_4	L_5	C_6	L_7

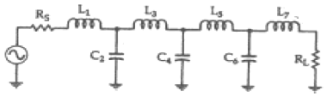


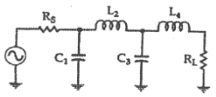Chebyshev Low-Pass Element Values for 0.01-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4
2	1.101	1.347	1.483		
	1.111	1.247	1.595		
	1.250	0.943	1.997		
	1.429	0.759	2.344		
	1.667	0.609	2.750		
	2.000	0.479	3.277		
	2.500	0.363	4.033		
	3.333	0.259	5.255		
	5.000	0.164	7.650		
	10.000	0.078	14.749		
	∞	1.412	0.742		
3	1.000	1.181	1.821	1.181	
	0.900	1.092	1.660	1.480	
	0.800	1.097	1.443	1.806	
	0.700	1.160	1.228	2.165	
	0.600	1.274	1.024	2.598	
	0.500	1.452	0.829	3.164	
	0.400	1.734	0.645	3.974	
	0.300	2.216	0.470	5.280	
	0.200	3.193	0.305	7.834	
	0.100	6.141	0.148	15.390	
	∞	1.501	1.433	0.591	
4	1.100	0.950	1.938	1.761	1.046
	1.111	0.854	1.946	1.744	1.165
	1.250	0.618	2.075	1.542	1.617
	1.429	0.495	2.279	1.334	2.008
	1.667	0.398	2.571	1.128	2.461
	2.000	0.316	2.994	0.926	3.045
	2.500	0.242	3.641	0.729	3.875
	3.333	0.174	4.727	0.538	5.209
	5.000	0.112	6.910	0.352	7.813
	10.000	0.054	13.469	0.173	15.510
	∞	1.529	1.694	1.312	0.523

n	R_L/R_S	L_1	C_2	L_3	C_4

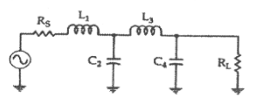


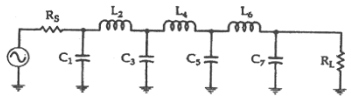Chebyshev Low-Pass Element Values for 0.01-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	1.000	0.977	1.685	2.037	1.685	0.977		
	0.900	0.880	1.456	2.174	1.641	1.274		
	0.800	0.877	1.235	2.379	1.499	1.607		
	0.700	0.926	1.040	2.658	1.323	1.977		
	0.600	1.019	0.863	3.041	1.135	2.424		
	0.500	1.166	0.699	3.584	0.942	3.009		
	0.400	1.398	0.544	4.403	0.749	3.845		
	0.300	1.797	0.398	5.772	0.557	5.193		
	0.200	2.604	0.259	8.514	0.368	7.826		
	0.100	5.041	0.127	16.741	0.182	15.613		
	∞	1.547	1.795	1.645	1.237	0.488		
6	1.101	0.851	1.796	1.841	2.027	1.631	0.937	
	1.111	0.760	1.782	1.775	2.094	1.638	1.053	
	1.250	0.545	1.864	1.489	2.403	1.507	1.504	
	1.429	0.436	2.038	1.266	2.735	1.332	1.899	
	1.667	0.351	2.298	1.061	3.167	1.145	2.357	
	2.000	0.279	2.678	0.867	3.768	0.954	2.948	
	2.500	0.214	3.261	0.682	4.667	0.761	3.790	
	3.333	0.155	4.245	0.503	6.163	0.568	5.143	
	5.000	0.100	6.223	0.330	9.151	0.376	7.785	
	10.000	0.048	12.171	0.162	18.105	0.187	15.595	
	∞	1.551	1.847	1.790	1.598	1.190	0.469	
7	1.000	0.913	1.595	2.002	1.870	2.002	1.595	0.913
	0.900	0.816	1.362	2.089	1.722	2.202	1.581	1.206
	0.800	0.811	1.150	2.262	1.525	2.465	1.464	1.538
	0.700	0.857	0.967	2.516	1.323	2.802	1.307	1.910
	0.600	0.943	0.803	2.872	1.124	3.250	1.131	2.359
	0.500	1.080	0.650	3.382	0.928	3.875	0.947	2.948
	0.400	1.297	0.507	4.156	0.735	4.812	0.758	3.790
	0.300	1.669	0.372	5.454	0.546	6.370	0.568	5.148
	0.200	2.242	0.242	8.057	0.360	9.484	0.378	7.802
	0.100	4.701	0.119	15.872	0.178	18.818	0.188	15.652
	∞	1.559	1.867	1.866	1.765	1.563	1.161	0.456

n	R_L/R_S	L_1	C_2	L_3	C_4	L_5	C_6	L_7

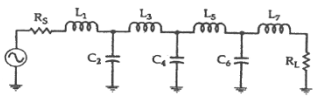


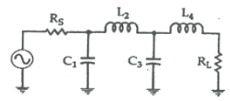Chebyshev Low-Pass Prototype Element Values for 0.1-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4
2	1.355	1.209	1.638		
	1.429	0.977	1.982		
	1.667	0.733	2.489		
	2.000	0.560	3.054		
	2.500	0.417	3.827		
	3.333	0.293	5.050		
	5.000	0.184	7.426		
	10.000	0.087	14.433		
	∞	1.391	0.819		
3	1.000	1.433	1.594	1.433	
	0.900	1.426	1.494	1.622	
	0.800	1.451	1.356	1.871	
	0.700	1.521	1.193	2.190	
	0.600	1.648	1.017	2.603	
	0.500	1.853	0.838	3.159	
	0.400	2.186	0.660	3.968	
	0.300	2.763	0.486	5.279	
	0.200	3.942	0.317	7.850	
	0.100	7.512	0.155	15.466	
	∞	1.513	1.510	0.716	
4	1.355	0.992	2.148	1.585	1.341
	1.429	0.779	2.348	1.429	1.700
	1.667	0.576	2.730	1.185	2.243
	2.000	0.440	3.227	0.967	2.856
	2.500	0.329	3.961	0.760	3.698
	3.333	0.233	5.178	0.560	5.030
	5.000	0.148	7.607	0.367	7.614
	10.000	0.070	14.887	0.180	15.230
	∞	1.511	1.768	1.455	0.673

n	R_L/R_S	L_1	C_2	L_3	C_4

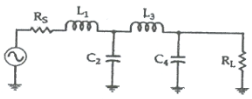


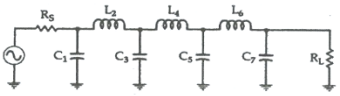Chebyshev Low-Pass Prototype Element Values for 0.1-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	1.000	1.301	1.556	2.241	1.556	1.301		
	0.900	1.285	1.433	2.380	1.488	1.488		
	0.800	1.300	1.282	2.582	1.382	1.738		
	0.700	1.358	1.117	2.868	1.244	2.062		
	0.600	1.470	0.947	3.269	1.085	2.484		
	0.500	1.654	0.778	3.845	0.913	3.055		
	0.400	1.954	0.612	4.720	0.733	3.886		
	0.300	2.477	0.451	6.196	0.550	5.237		
	0.200	3.546	0.295	9.127	0.366	7.889		
	0.100	6.787	0.115	17.957	0.182	15.745		
	∞	1.561	1.807	1.766	1.417	0.651		
6	1.355	0.942	2.080	1.659	2.247	1.534	1.277	
	1.429	0.735	2.249	1.454	2.544	1.405	1.629	
	1.667	0.542	2.600	1.183	3.064	1.185	2.174	
	2.000	0.414	3.068	0.958	3.712	0.979	2.794	
	2.500	0.310	3.765	0.749	4.651	0.778	3.645	
	3.333	0.220	4.927	0.551	6.195	0.580	4.996	
	5.000	0.139	7.250	0.361	9.261	0.384	7.618	
	10.000	0.067	14.220	0.178	18.427	0.190	15.350	
	∞	1.534	1.884	1.831	1.749	1.394	0.638	
7	1.000	1.262	1.520	2.239	1.680	2.239	1.520	1.262
	0.900	1.242	1.395	2.361	1.578	2.397	1.459	1.447
	0.800	1.255	1.245	2.548	1.443	2.624	1.362	1.697
	0.700	1.310	1.083	2.819	1.283	2.942	1.233	2.021
	0.600	1.417	0.917	3.205	1.209	3.384	1.081	2.444
	0.500	1.595	0.753	3.764	0.928	4.015	0.914	3.018
	0.400	1.885	0.593	4.618	0.742	4.970	0.738	3.855
	0.300	2.392	0.437	6.054	0.556	6.569	0.557	5.217
	0.200	3.428	0.286	8.937	0.369	9.770	0.372	7.890
	0.100	6.570	0.141	17.603	0.184	19.376	0.186	15.813
	∞	1.575	1.858	1.921	1.827	1.734	1.379	0.631

n	R_L/R_S	L_1	C_2	L_3	C_4	L_5	C_6	L_7

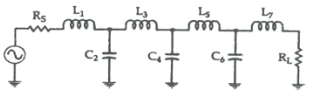


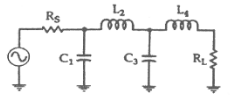Chebyshev Low-Pass Prototype Element Values for 0.5-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4
2	1.984	0.983	1.950		
	2.000	0.909	2.103		
	2.500	0.564	3.165		
	3.333	0.375	4.411		
	5.000	0.228	6.700		
	10.000	0.105	13.322		
	∞	1.307	0.975		
3	1.000	1.864	1.280	1.834	
	0.900	1.918	1.209	2.026	
	0.800	1.997	1.120	2.237	
	0.700	2.114	1.015	2.517	
	0.500	2.557	0.759	3.436	
	0.400	2.985	0.615	4.242	
	0.300	3.729	0.463	5.576	
	0.200	5.254	0.309	8.225	
	0.100	9.890	0.153	16.118	
	∞	1.572	1.518	0.932	
4	1.984	0.920	2.586	1.304	1.826
	2.000	0.845	2.720	1.238	1.985
	2.500	0.516	3.766	0.869	3.121
	3.333	0.344	5.120	0.621	4.480
	5.000	0.210	7.708	0.400	6.987
	10.000	0.098	15.352	0.194	14.262
	∞	1.436	1.889	1.521	0.913

n	R_L/R_S	L_1	C_2	L_3	C_4

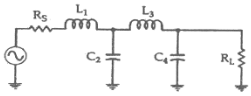

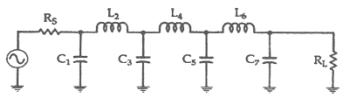Chebyshev Low-Pass Prototype Element Values for 0.5-dB Ripple



n	R_S/R_L	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	1.000	1.807	1.303	2.691	1.303	1.807		
	0.900	1.854	1.222	2.849	1.238	1.970		
	0.800	1.926	1.126	3.060	1.157	2.185		
	0.700	2.035	1.015	3.353	1.058	2.470		
	0.600	2.200	0.890	3.765	0.942	2.861		
	0.500	2.457	0.754	4.367	0.810	3.414		
	0.400	2.870	0.609	5.296	0.664	4.245		
	0.300	3.588	0.459	6.871	0.508	5.625		
	0.200	5.064	0.306	10.054	0.343	8.367		
	0.100	9.556	0.153	19.647	0.173	16.574		
	∞	1.630	1.740	1.922	1.514	0.903		
6	1.984	0.905	2.577	1.368	2.713	1.299	1.796	
	2.000	0.830	2.704	1.291	2.872	1.237	1.956	
	2.500	0.506	3.722	0.890	4.109	0.881	3.103	
	3.333	0.337	5.055	0.632	5.699	0.635	4.481	
	5.000	0.206	7.615	0.406	8.732	0.412	7.031	
	10.000	0.096	15.186	0.197	17.681	0.202	14.433	
	∞	1.790	1.296	2.718	1.385	2.718	1.296	1.790
7	1.000	1.835	1.215	2.869	1.308	2.883	1.234	1.953
	0.900	1.905	1.118	3.076	1.215	3.107	1.155	2.168
	0.800	2.011	1.007	3.364	1.105	3.416	1.058	2.455
	0.700	2.174	0.882	3.772	0.979	3.852	0.944	2.848
	0.600	2.428	0.747	4.370	0.838	2.289	0.814	3.405
	0.500	2.835	0.604	5.295	0.685	5.470	0.669	4.243
	0.400	3.546	0.455	6.867	0.522	7.134	0.513	5.635
	0.300	5.007	0.303	10.049	0.352	10.496	0.348	8.404
	0.200	9.456	0.151	19.649	0.178	20.631	0.176	16.665
	0.100	1.646	1.777	2.031	1.789	1.924	1.503	0.895
	∞							

n	R_L/R_S	L_1	C_2	L_3	C_4	L_5	C_6	L_7

