ELEC70051
EE9-AO6

IMPERIAL COLLEGE LONDON

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
EXAMINATIONS

MSc and EEE PART IV: MEng and ACGI

RADIO FREQUENCY SUBSYSTEMS

Tuesday, 6 May 2025, 10:00 AM

Time allowed: 3:00 hours

There are FOUR questions on this paper.

Answer Question ONE and any TWO out of the remaining three questions.

Question ONE is COMPULSARY and carries a weighting of 50%. The remaining questions carry a weighting of 25% each.

This is an OPEN BOOK examination.

Any special instructions for invigilators and information for candidates are on page 1.

Examiners responsible First Marker(s) : S. Lucyszyn
Second Marker(s) : W.T. Pike

© Imperial College London

Special instructions for invigilators

This is an OPEN BOOK examination.

Special instructions for students

There are 4 (four) questions in total.

Question 1 is COMPULSARY and carries a weighting of 50%.

Answer 2 (two) out of the remaining 3 (three) questions, each carrying a weighting of 25%.

All variables and acronyms have their usual meaning.

1.

(a) Using a signal flow graph or otherwise, derive an expression for the input voltage-wave reflection coefficient for a 2-port network that is terminated with a load impedance Z_L in terms of the network's S-parameters.

[10]

(b) From the expression derived in 1(a), describe how stability circles can be created on the Smith chart. What does this stability circle represent when it encompasses the normalised impedance matched, z_0, point on the Smith chart and when it does not encompass this point?

[5]

(c) Given a 2-port network with the following S-parameters:

$$[S] = \begin{bmatrix} 0.5 & 0.5 \\ 10 & 0.5 \end{bmatrix} \qquad (1.1)$$

What is the input voltage-wave reflection coefficient if the output port is terminated with a load impedance Z_L = -5 Ω and a reference impedance Z_0 = 50 Ω?

[5]

(d) For the 2-port network given in 1(c) the Rollett's stability factor is 2.3. Comment on the apparent contradiction between the Rollett's stability factor and the input voltage-wave reflection coefficient found in 1(c). What is the maximum gain that can be achieved with a passive load impedance termination?

[5]

(e) Draw the topology of a double-balanced amplifier.

[5]

(f) If 3 dB quadrature couplers are used in conjunction with identical non-ideal single-ended amplifiers, use S-parameter analysis to determine expressions for the overall insertion gain and input return loss. Assume the couplers are perfectly matched to the reference impedance, Z_0, and the interconnections between the main components are ideal.

[10]

(g) For the topology in 1(e), if the working single-ended amplifiers have a forward voltage wave transmission coefficient of S_{21} = |10|∠35°, determine the overall insertion gain and input return loss if one of the amplifiers fails, such that S_{21} = 0. Assume that there is no change in the input or output impedances of the failed transistor. What is the main application of this topology and what are its advantages and disadvantages when compared to a single-ended amplifier?

[10]

2.

(a) Electromagnetic radiation can cause heating of biological tissue via two main phenomena: dielectric heating and Joule heating.

i) Briefly explain the mechanism behind dielectric heating.

[2]

ii) Briefly explain the mechanism behind Joule heating.

[2]

(b) The relative effective dielectric permittivity (also known as the dielectric constant) of certain biological tissues can be characterized by a Debye model. Table 2 shows the coefficients for a single-pole Debye model describing human body tissue from 1 MHz to 10 GHz:

Table 2: Single-pole Debye model coefficients.

ε_∞	σ_0 [S/m]	$\Delta\varepsilon_1$	τ_1 [s]
20	0	20	$\frac{1}{2\pi \cdot 100 \cdot 10^6}$

i) Derive an algebraic expression for the real part of the relative effective dielectric permittivity ($\varepsilon_{r\,eff}{}'$) for a one-pole Debye model.

[3]

ii) Derive an algebraic expression for the imaginary part of the relative effective dielectric permittivity ($\varepsilon_{r\,eff}{}''$) for a one-pole Debye model.

[1]

iii) Sketch the real and imaginary parts of the relative effective dielectric permittivity using the data from Table 2 on a log-frequency axis, labelling the key points.

[8]

(c) A mobile phone is undergoing SAR testing for use in the United States. The peak average SAR is measured to be 3 W/kg, averaged over a volume of 1.92 cm^3.

i) What is the FCC limit on average SAR?

[2]

ii) The tissue has a mass volume density of 1,040 kg/m^3. What is the mass that the average SAR has been averaged over?

[2]

iii) Give two reasons why this mobile phone may not comply with the FCC limit. *Hint: Consider the averaging volumes or masses.*

[2]

iv) State a scenario in which absorbed electromagnetic power can be SAR-compliant but still be harmful to humans.

[1]

v) Calculate the maximum theoretical temperature change, assuming constant irradiation for 10 mins, given a specific heat capacity of 3,600 J/kg/°C.

[2]

3.

(a) Given a square wave signal generator, with a clock frequency that can vary between zero and 1.0 GHz, propose how this could be used to generate a sinusoidal signal at a frequency of 1.8 GHz. *Hint: Consider the Fourier series of the square wave.*

[5]

(b) Design a lumped-element *L*-*C* high-pass filter to meet the following specifications:

Pass band attenuation ripple	0.1 dB
-3 dB cut-off frequency:	1,500 MHz
Stop band frequency:	600 MHz
Stop band attenuation:	> 70 dB
Source impedance, Z_S:	50 Ω
Load impedance, Z_L:	50 Ω


[10]

(c) Determine the worst-case levels of return losses within both the pass band and the stop band for the filter in 3(b). How could the stop band return loss adversely affect the implementation of 3(a)? Suggest a suitable topology for overcoming this problem.

[10]

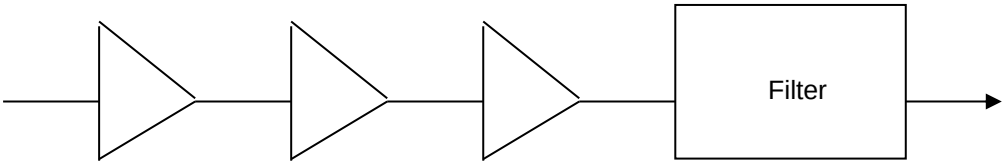4.

An amplifier chain is illustrated in Figure 4.1. All sub-systems are assumed to be perfectly impedance matched.



G = 15 dB	G = 8 dB	G = 4 dB	G = -0.7 dB
$IP3$ = 30 dBm	$IP3$ = 40 dBm	$IP3$ = 50 dBm	
F = 1 dB	F = 2 dB	F = 3 dB	

Figure 4.1

For an overall input power of +3 dBm, calculate the following at the output of each sub-system:-

(i) C [2]

(ii) IP_3 [8]


(iii) IMD_3 [3]

(iv) I_3 [2]


(v) Overall F [10]

All variables have their usual meaning.


Standard Filter Curves and Tables

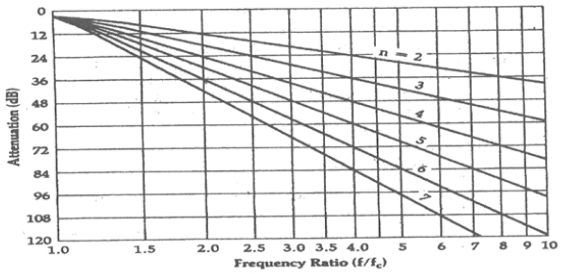

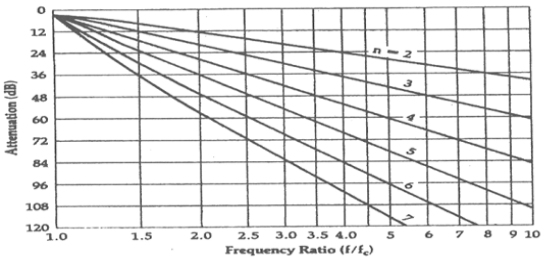
Attenuation characteristics for Butterworth filters.



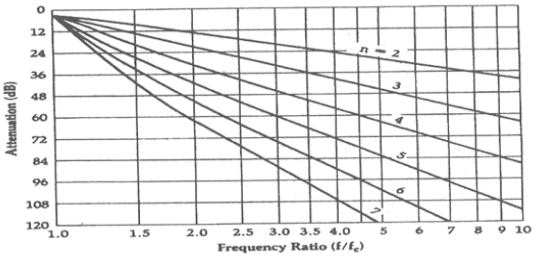
Attenuation characteristics for a Chebyshev filter with 0.01-dB ripple.



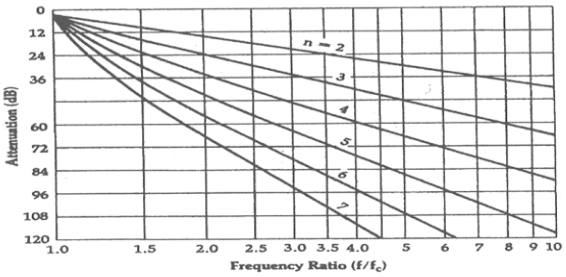Attenuation characteristics for a Chebyshev filter with 0.1-dB ripple.




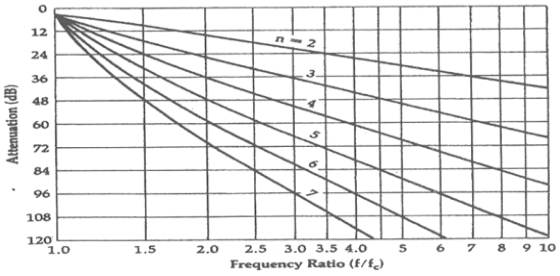Attenuation characteristics for a Chebyshev filter with 0.5-dB ripple.




Attenuation characteristics for a Chebyshev filter with 1-dB ripple.

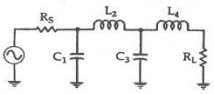Chebyshev Low-Pass Prototype Element Values for 1.0-dB Ripple




R_S/R_L	C_1	L_2	C_3	L_4
3.000	0.572	3.132		
4.000	0.365	4.600		
8.000	0.157	9.658		
∞	1.213	1.109		
1.000	2.216	1.088	2.216	
0.500	4.431	0.817	2.216	
0.333	6.647	0.726	2.216	
0.250	8.862	0.680	2.216	
0.125	17.725	0.612	2.216	
∞	1.652	1.460	1.108	
3.000	0.653	4.411	0.814	2.535
4.000	0.452	7.083	0.612	2.848
8.000	0.209	17.164	0.428	3.281
∞	1.350	2.010	1.488	1.106

R_L/R_S	L_1	C_2	L_3	C_4

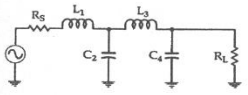


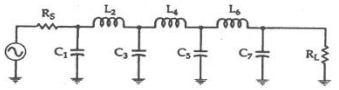Chebyshev Low-Pass Prototype Element Values for 1.0-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	1.000	2.207	1.128	3.103	1.128	2.207		
	0.500	4.414	0.565	4.653	1.128	2.207		
	0.333	6.622	0.376	6.205	1.128	2.207		
	0.250	8.829	0.282	7.756	1.128	2.207		
	0.125	17.657	0.141	13.961	1.128	2.207		
	∞	1.721	1.645	2.061	1.493	1.103		
6	3.000	0.679	3.873	0.771	4.711	0.969	2.406	
	4.000	0.481	5.644	0.476	7.351	0.849	2.582	
	8.000	0.227	12.310	0.198	16.740	0.726	2.800	
	∞	1.378	2.097	1.690	2.074	1.494	1.102	
7	1.000	2.204	1.131	3.147	1.194	3.147	1.131	2.204
	0.500	4.408	0.566	6.293	0.895	3.147	1.131	2.204
	0.333	6.612	0.377	9.441	0.798	3.147	1.131	2.204
	0.250	8.815	0.283	12.588	0.747	3.147	1.131	2.204
	0.125	17.631	0.141	25.175	0.671	3.147	1.131	2.204
	∞	1.741	1.677	2.155	1.703	2.079	1.494	1.102

n	R_L/R_S	L_1	C_2	L_3	C_4	L_5	C_6	L_7

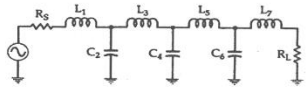


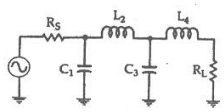Butterworth Low-Pass Prototype Element Values




n	R_S/R_L	C_1	L_2	C_3	L_4
2	1.111	1.035	1.835		
	1.250	0.849	2.121		
	1.429	0.697	2.439		
	1.667	0.566	2.828		
	2.000	0.448	3.346		
	2.500	0.342	4.095		
	3.333	0.245	5.313		
	5.000	0.156	7.707		
	10.000	0.074	14.814		
	∞	1.414	0.707		
3	0.900	0.808	1.633	1.599	
	0.800	0.844	1.384	1.926	
	0.700	0.915	1.165	2.277	
	0.600	1.023	0.965	2.702	
	0.500	1.181	0.779	3.261	
	0.400	1.425	0.604	4.064	
	0.300	1.838	0.440	5.363	
	0.200	2.669	0.284	7.910	
	0.100	5.167	0.138	15.455	
	∞	1.500	1.333	0.500	
4	1.111	0.466	1.592	1.744	1.469
	1.250	0.388	1.695	1.511	1.811
	1.429	0.325	1.862	1.291	2.175
	1.667	0.269	2.103	1.082	2.613
	2.000	0.218	2.452	0.883	3.187
	2.500	0.169	2.986	0.691	4.009
	3.333	0.124	3.883	0.507	5.338
	5.000	0.080	5.684	0.331	7.940
	10.000	0.039	11.064	0.162	15.642
	∞	1.531	1.577	1.082	0.383

n	R_L/R_S	L_1	C_2	L_3	C_4

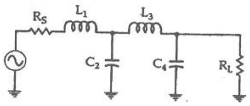


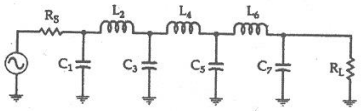Butterworth Low-Pass Prototype Element Values




n	R_S/R_L	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	0.900	0.442	1.027	1.910	1.756	1.389		
	0.800	0.470	0.866	2.061	1.544	1.738		
	0.700	0.517	0.731	2.285	1.333	2.108		
	0.600	0.586	0.609	2.600	1.126	2.552		
	0.500	0.686	0.496	3.051	0.924	3.133		
	0.400	0.838	0.388	3.736	0.727	3.965		
	0.300	1.094	0.285	4.884	0.537	5.307		
	0.200	1.608	0.186	7.185	0.352	7.935		
	0.100	3.512	0.091	14.095	0.173	15.710		
	∞	1.545	1.694	1.382	0.894	0.309		
6	1.111	0.289	1.040	1.322	2.054	1.744	1.335	
	1.250	0.245	1.116	1.126	2.239	1.550	1.688	
	1.429	0.207	1.236	0.957	2.499	1.346	2.062	
	1.667	0.173	1.407	0.801	2.858	1.143	2.509	
	2.000	0.141	1.653	0.654	3.369	0.942	3.094	
	2.500	0.111	2.028	0.514	4.141	0.745	3.931	
	3.333	0.082	2.656	0.379	5.433	0.552	5.280	
	5.000	0.054	3.917	0.248	8.020	0.363	7.922	
	10.000	0.026	7.705	0.122	15.786	0.179	15.738	
	∞	1.553	1.759	1.553	1.202	0.758	0.259	
7	0.900	0.299	0.711	1.404	1.489	2.125	1.727	1.296
	0.800	0.322	0.606	1.517	1.278	2.334	1.546	1.652
	0.700	0.357	0.515	1.688	1.091	2.618	1.350	2.028
	0.600	0.408	0.432	1.928	0.917	3.005	1.150	2.477
	0.500	0.480	0.354	2.273	0.751	3.553	0.951	3.064
	0.400	0.590	0.278	2.795	0.592	4.380	0.754	3.904
	0.300	0.775	0.206	3.671	0.437	5.761	0.560	5.258
	0.200	1.145	0.135	5.427	0.287	8.526	0.369	7.908
	0.100	2.257	0.067	10.700	0.142	16.822	0.182	15.748
	∞	1.558	1.799	1.659	1.397	1.055	0.656	0.223

n	R_L/R_S	L_1	C_2	L_3	C_4	L_5	C_6	L_7

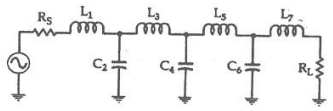


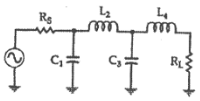Chebyshev Low-Pass Element Values for 0.01-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4
2	1.101	1.347	1.483		
	1.111	1.247	1.595		
	1.250	0.943	1.997		
	1.429	0.759	2.344		
	1.667	0.609	2.750		
	2.000	0.479	3.277		
	2.500	0.363	4.033		
	3.333	0.259	5.255		
	5.000	0.164	7.650		
	10.000	0.078	14.749		
	∞	1.412	0.742		
3	1.000	1.181	1.821	1.181	
	0.900	1.092	1.660	1.480	
	0.800	1.097	1.443	1.806	
	0.700	1.160	1.228	2.165	
	0.600	1.274	1.024	2.598	
	0.500	1.452	0.829	3.164	
	0.400	1.734	0.645	3.974	
	0.300	2.216	0.470	5.280	
	0.200	3.193	0.305	7.834	
	0.100	6.141	0.148	15.390	
	∞	1.501	1.433	0.591	
4	1.100	0.950	1.938	1.761	1.046
	1.111	0.854	1.946	1.744	1.165
	1.250	0.618	2.075	1.542	1.617
	1.429	0.495	2.279	1.334	2.008
	1.667	0.398	2.571	1.128	2.461
	2.000	0.316	2.994	0.926	3.045
	2.500	0.242	3.641	0.729	3.875
	3.333	0.174	4.727	0.538	5.209
	5.000	0.112	6.910	0.352	7.813
	10.000	0.054	13.469	0.173	15.510
	∞	1.529	1.694	1.312	0.523

n	R_L/R_S	L_1	C_2	L_3	C_4

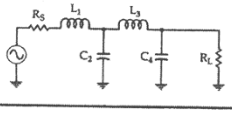


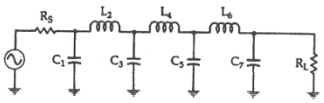Chebyshev Low-Pass Element Values for 0.01-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	1.000	0.977	1.685	2.037	1.685	0.977		
	0.900	0.880	1.456	2.174	1.641	1.274		
	0.800	0.877	1.235	2.379	1.499	1.607		
	0.700	0.926	1.040	2.658	1.323	1.977		
	0.600	1.019	0.863	3.041	1.135	2.424		
	0.500	1.166	0.699	3.584	0.942	3.009		
	0.400	1.398	0.544	4.403	0.749	3.845		
	0.300	1.797	0.398	5.772	0.557	5.193		
	0.200	2.604	0.259	8.514	0.368	7.826		
	0.100	5.041	0.127	16.741	0.182	15.613		
	∞	1.547	1.795	1.645	1.237	0.488		
6	1.101	0.851	1.796	1.841	2.027	1.631	0.937	
	1.111	0.760	1.782	1.775	2.094	1.638	1.053	
	1.250	0.545	1.864	1.489	2.403	1.507	1.504	
	1.429	0.436	2.038	1.266	2.735	1.332	1.899	
	1.667	0.351	2.298	1.061	3.167	1.145	2.357	
	2.000	0.279	2.678	0.867	3.768	0.954	2.948	
	2.500	0.214	3.261	0.682	4.667	0.761	3.790	
	3.333	0.155	4.245	0.503	6.163	0.568	5.143	
	5.000	0.100	6.223	0.330	9.151	0.376	7.785	
	10.000	0.048	12.171	0.162	18.105	0.187	15.595	
	∞	1.551	1.847	1.790	1.598	1.190	0.469	
7	1.000	0.913	1.595	2.002	1.870	2.002	1.595	0.913
	0.900	0.816	1.362	2.089	1.722	2.202	1.581	1.206
	0.800	0.811	1.150	2.262	1.525	2.465	1.464	1.538
	0.700	0.857	0.967	2.516	1.323	2.802	1.307	1.910
	0.600	0.943	0.803	2.872	1.124	3.250	1.131	2.359
	0.500	1.080	0.650	3.382	0.928	3.875	0.947	2.948
	0.400	1.297	0.507	4.156	0.735	4.812	0.758	3.790
	0.300	1.669	0.372	5.454	0.546	6.370	0.568	5.148
	0.200	2.242	0.242	8.057	0.360	9.484	0.378	7.802
	0.100	4.701	0.119	15.872	0.178	18.818	0.188	15.652
	∞	1.559	1.867	1.866	1.765	1.563	1.161	0.456

n	R_L/R_S	L_1	C_2	L_3	C_4	L_5	C_6	L_7

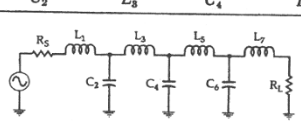


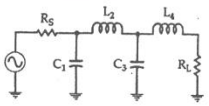Chebyshev Low-Pass Prototype Element Values for 0.1-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4
2	1.355	1.209	1.638		
	1.429	0.977	1.982		
	1.667	0.733	2.489		
	2.000	0.560	3.054		
	2.500	0.417	3.827		
	3.333	0.293	5.050		
	5.000	0.184	7.426		
	10.000	0.087	14.433		
	∞	1.391	0.819		
3	1.000	1.433	1.594	1.433	
	0.900	1.426	1.494	1.622	
	0.800	1.451	1.356	1.871	
	0.700	1.521	1.193	2.190	
	0.600	1.648	1.017	2.603	
	0.500	1.853	0.838	3.159	
	0.400	2.186	0.660	3.968	
	0.300	2.763	0.486	5.279	
	0.200	3.942	0.317	7.850	
	0.100	7.512	0.155	15.466	
	∞	1.513	1.510	0.716	
4	1.355	0.992	2.148	1.585	1.341
	1.429	0.779	2.348	1.429	1.700
	1.667	0.576	2.730	1.185	2.243
	2.000	0.440	3.227	0.967	2.856
	2.500	0.329	3.961	0.760	3.698
	3.333	0.233	5.178	0.560	5.030
	5.000	0.148	7.607	0.367	7.614
	10.000	0.070	14.887	0.180	15.230
	∞	1.511	1.768	1.455	0.673

n	R_L/R_S	L_1	C_2	L_3	C_4

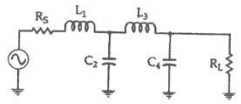


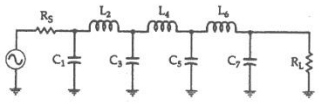Chebyshev Low-Pass Prototype Element Values for 0.1-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	1.000	1.301	1.556	2.241	1.556	1.301		
	0.900	1.285	1.433	2.380	1.488	1.488		
	0.800	1.300	1.282	2.582	1.382	1.738		
	0.700	1.358	1.117	2.868	1.244	2.062		
	0.600	1.470	0.947	3.269	1.085	2.484		
	0.500	1.654	0.778	3.845	0.913	3.055		
	0.400	1.954	0.612	4.720	0.733	3.886		
	0.300	2.477	0.451	6.196	0.550	5.237		
	0.200	3.546	0.295	9.127	0.366	7.889		
	0.100	6.787	0.115	17.957	0.182	15.745		
	∞	1.561	1.807	1.766	1.417	0.651		
6	1.355	0.942	2.080	1.659	2.247	1.534	1.277	
	1.429	0.735	2.249	1.454	2.544	1.405	1.629	
	1.667	0.542	2.600	1.183	3.064	1.185	2.174	
	2.000	0.414	3.068	0.958	3.712	0.979	2.794	
	2.500	0.310	3.765	0.749	4.651	0.778	3.645	
	3.333	0.220	4.927	0.551	6.195	0.580	4.996	
	5.000	0.139	7.250	0.361	9.261	0.384	7.618	
	10.000	0.067	14.220	0.178	18.427	0.190	15.350	
	∞	1.534	1.884	1.831	1.749	1.394	0.638	
7	1.000	1.262	1.520	2.239	1.680	2.239	1.520	1.262
	0.900	1.242	1.395	2.361	1.578	2.397	1.459	1.447
	0.800	1.255	1.245	2.548	1.443	2.624	1.362	1.697
	0.700	1.310	1.083	2.819	1.283	2.942	1.233	2.021
	0.600	1.417	0.917	3.205	1.209	3.384	1.081	2.444
	0.500	1.595	0.753	3.764	0.928	4.015	0.914	3.018
	0.400	1.885	0.593	4.618	0.742	4.970	0.738	3.855
	0.300	2.392	0.437	6.054	0.556	6.569	0.557	5.217
	0.200	3.428	0.286	8.937	0.369	9.770	0.372	7.890
	0.100	6.570	0.141	17.603	0.184	19.376	0.186	15.813
	∞	1.575	1.858	1.921	1.827	1.734	1.379	0.631

n	R_L/R_S	L_1	C_2	L_3	C_4	L_5	C_6	L_7

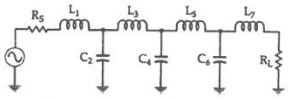


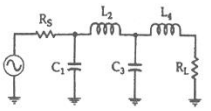Chebyshev Low-Pass Prototype Element Values for 0.5-dB Ripple




n	R_S/R_L	C_1	L_2	C_3	L_4
2	1.984	0.983	1.950		
	2.000	0.909	2.103		
	2.500	0.564	3.165		
	3.333	0.375	4.411		
	5.000	0.228	6.700		
	10.000	0.105	13.322		
	∞	1.307	0.975		
3	1.000	1.864	1.280	1.834	
	0.900	1.918	1.209	2.026	
	0.800	1.997	1.120	2.237	
	0.700	2.114	1.015	2.517	
	0.500	2.557	0.759	3.436	
	0.400	2.985	0.615	4.242	
	0.300	3.729	0.463	5.576	
	0.200	5.254	0.309	8.225	
	0.100	9.890	0.153	16.118	
	∞	1.572	1.518	0.932	
4	1.984	0.920	2.586	1.304	1.826
	2.000	0.845	2.720	1.238	1.985
	2.500	0.516	3.766	0.869	3.121
	3.333	0.344	5.120	0.621	4.480
	5.000	0.210	7.708	0.400	6.987
	10.000	0.098	15.352	0.194	14.262
	∞	1.436	1.889	1.521	0.913

n	R_L/R_S	L_1	C_2	L_3	C_4

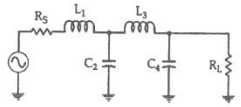

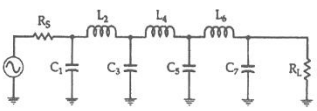Chebyshev Low-Pass Prototype Element Values for 0.5-dB Ripple



n	R_S/R_L	C_1	L_2	C_3	L_4	C_5	L_6	C_7
5	1.000	1.807	1.303	2.691	1.303	1.807		
	0.900	1.854	1.222	2.849	1.238	1.970		
	0.800	1.926	1.126	3.060	1.157	2.185		
	0.700	2.035	1.015	3.353	1.058	2.470		
	0.600	2.200	0.890	3.765	0.942	2.861		
	0.500	2.457	0.754	4.367	0.810	3.414		
	0.400	2.870	0.609	5.296	0.664	4.245		
	0.300	3.588	0.459	6.871	0.508	5.625		
	0.200	5.064	0.306	10.054	0.343	8.367		
	0.100	9.556	0.153	19.647	0.173	16.574		
	∞	1.630	1.740	1.922	1.514	0.903		
6	1.984	0.905	2.577	1.368	2.713	1.299	1.796	
	2.000	0.830	2.704	1.291	2.872	1.237	1.956	
	2.500	0.506	3.722	0.890	4.109	0.881	3.103	
	3.333	0.337	5.055	0.632	5.699	0.635	4.481	
	5.000	0.206	7.615	0.406	8.732	0.412	7.031	
	10.000	0.096	15.186	0.197	17.681	0.202	14.433	
7	1.000	1.790	1.296	2.718	1.385	2.718	1.296	1.790
	0.900	1.835	1.215	2.869	1.308	2.883	1.234	1.953
	0.800	1.905	1.118	3.076	1.215	3.107	1.155	2.168
	0.700	2.011	1.007	3.364	1.105	3.416	1.058	2.455
	0.600	2.174	0.882	3.772	0.979	3.852	0.944	2.848
	0.500	2.428	0.747	4.370	0.838	2.289	0.814	3.405
	0.400	2.835	0.604	5.295	0.685	5.470	0.669	4.243
	0.300	3.546	0.455	6.867	0.522	7.134	0.513	5.635
	0.200	5.007	0.303	10.049	0.352	10.496	0.348	8.404
	0.100	9.456	0.151	19.649	0.178	20.631	0.176	16.665
	∞	1.646	1.777	2.031	1.789	1.924	1.503	0.895

n	R_L/R_S	L_1	C_2	L_3	C_4	L_5	C_6	L_7

